

EE214 HomeWork Assignment


August 15,2024

Dev Arora
23B1271

4-bit Adder Subtractor


PenPaper Design:

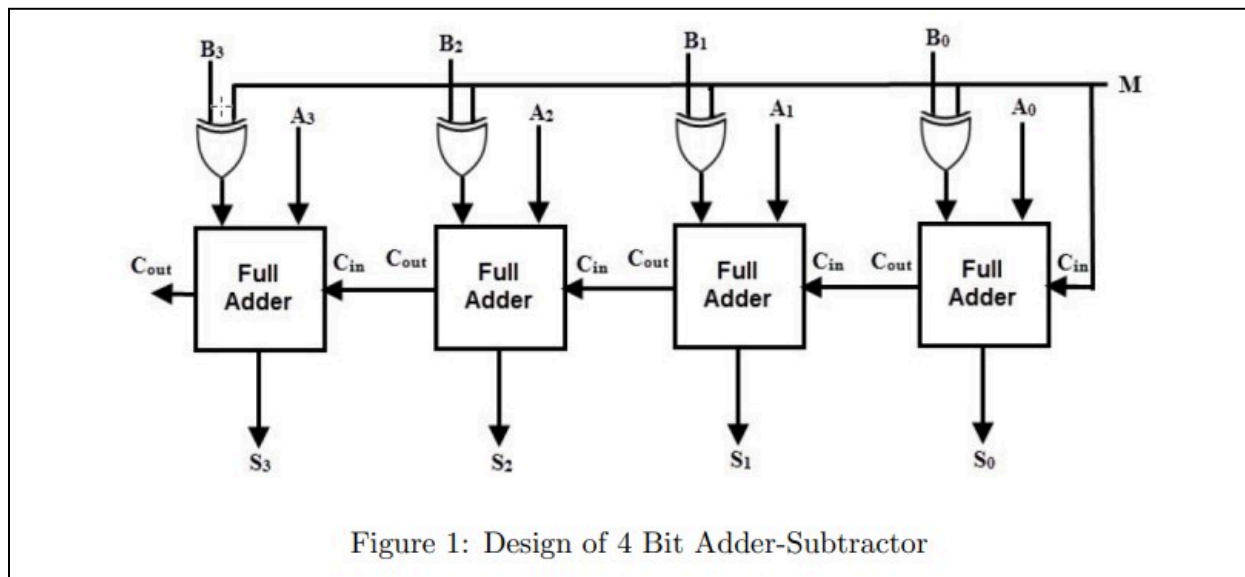- The Pen Paper Design was given in the assignment itself, i didn't draw it in my notebook, instead i used this given design itself.



Netlist:

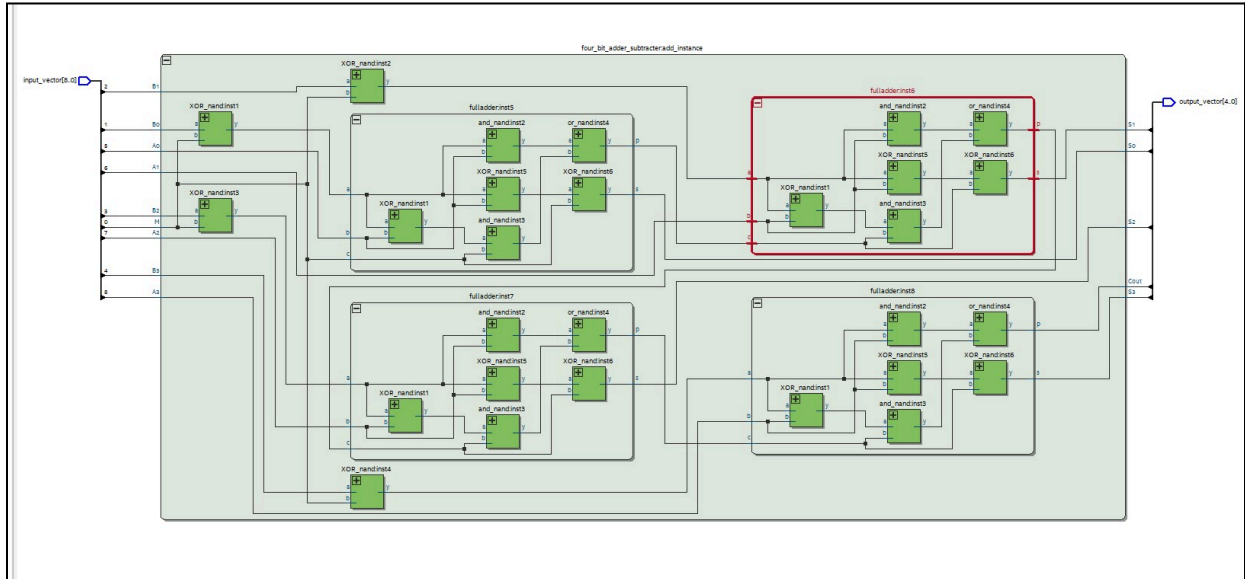- Shown below is the netlist of my code architecture. I have used XOR gate and Fulladder made by me earlier in this code.



Wave Simulation:

- The Wave Simulation of my 4 bit adder subtractor is attached below. All test cases passed(Success).

