

DIGITAL CIRCUITS LAB

EXP-2

August 25,2024

~Dev Arora
23B1271

Pen-Paper Design:

22/8/24

Page No.:


YOUVA

Date:


III. (WEEK-3) DESIGNING ENCODERS

PART A:-

* (4 to 2 encoder)

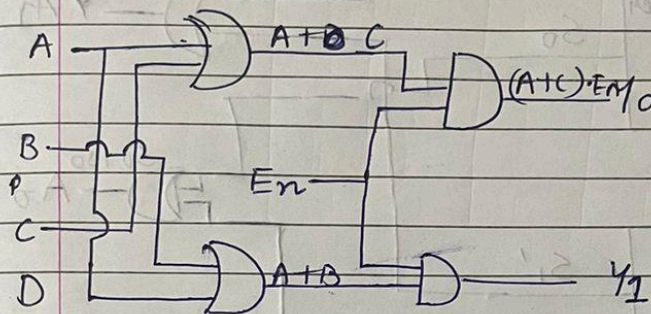


* PART-B (4 to 2 Priority Encoder)

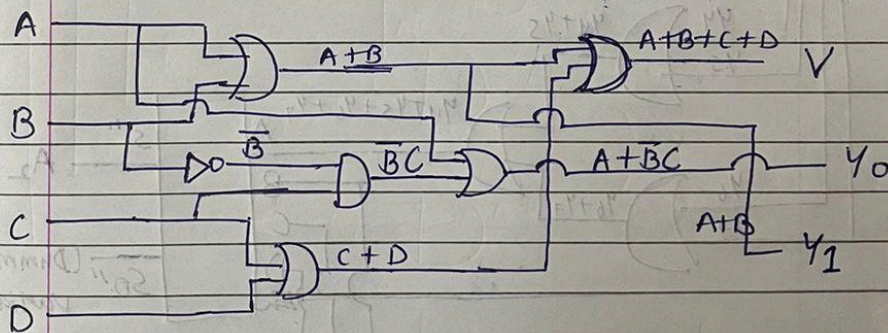



Amal

* PART C:- (8 to 3 priority encoder)


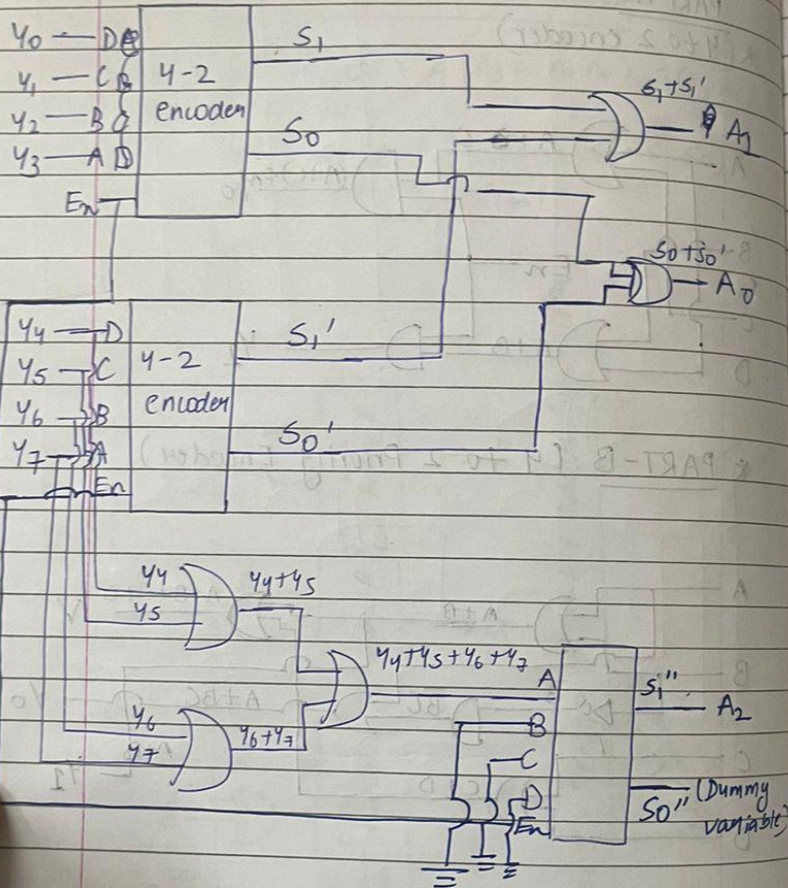


Completed

4 to 2 encoder:

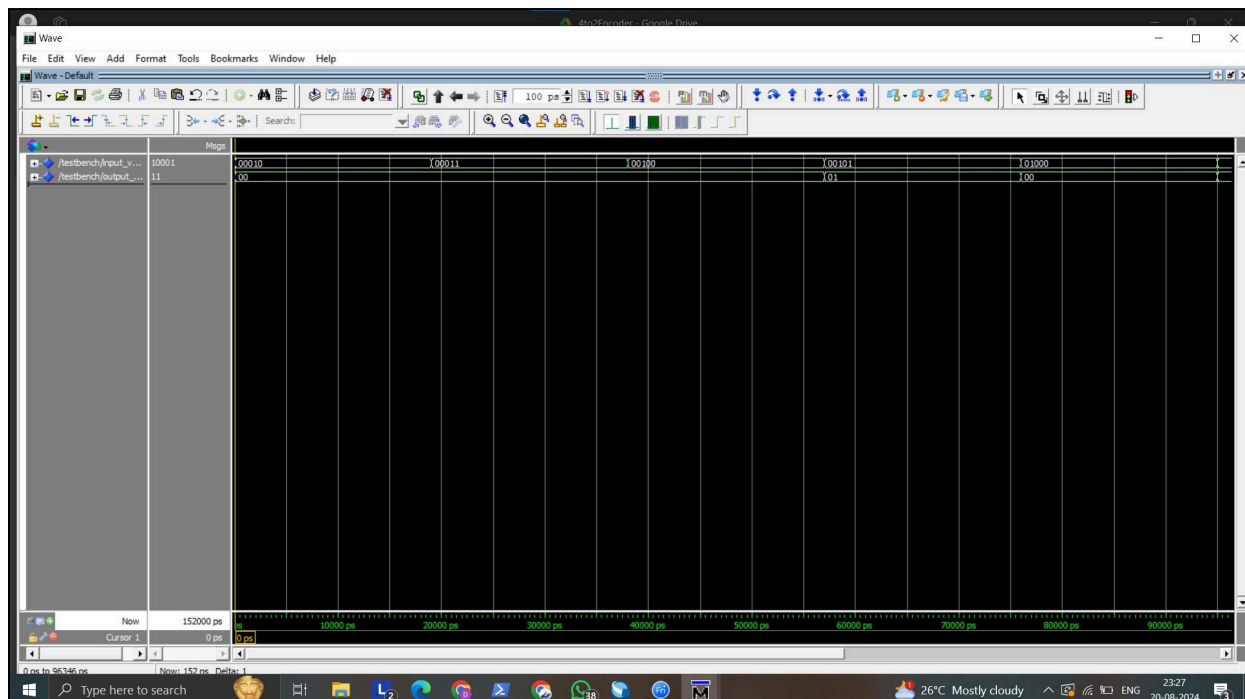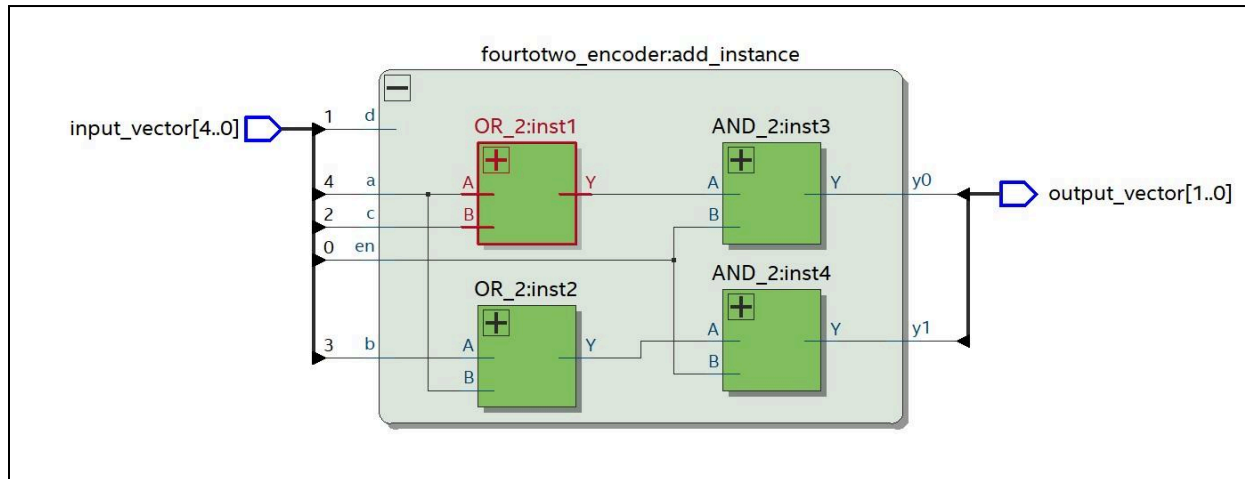

4 to 2 priority encoder:

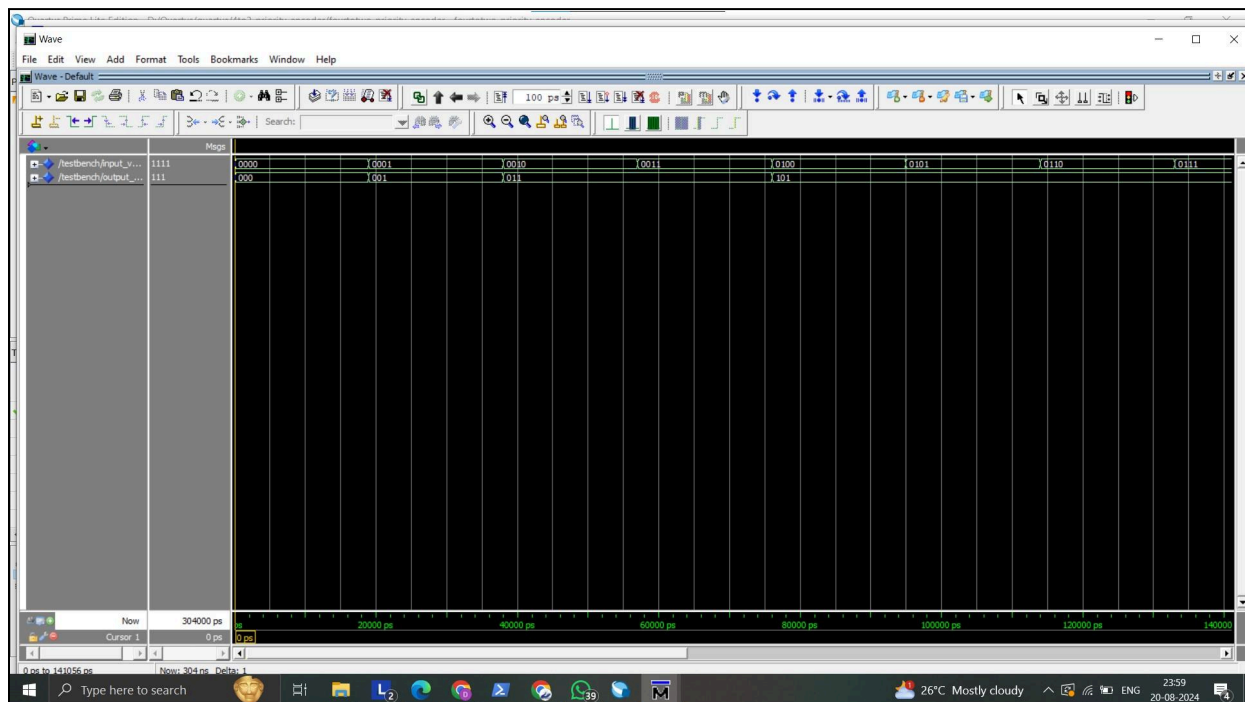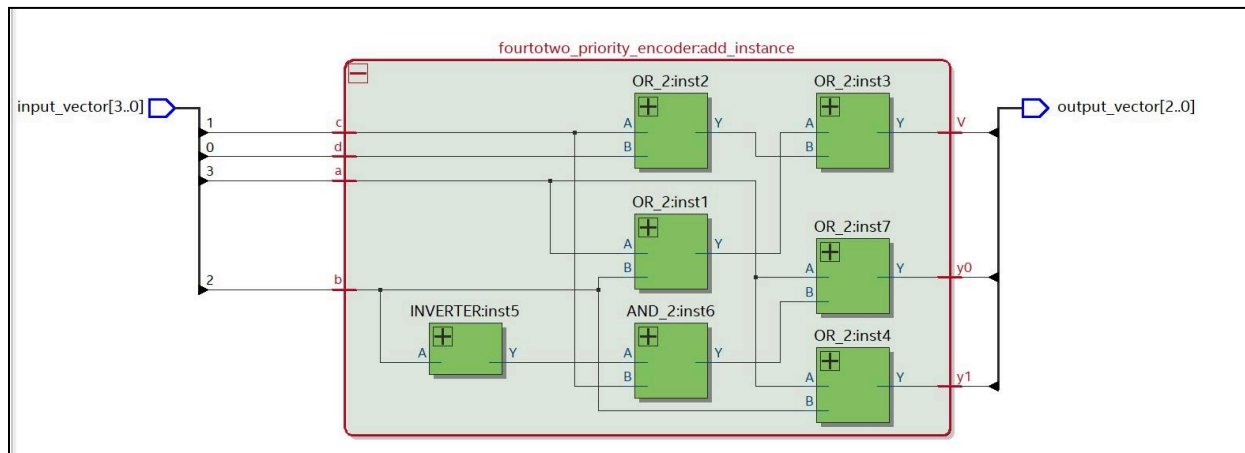

8 to 3 encoder:

